

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 1, 2019/2020

EEE 3156 DIGITAL SYSTEM
(EE Group)

21 OCTOBER 2019

9:00 AM – 11:00 AM
(2 Hours)

INSTRUCTION TO STUDENT

1. This Question paper consists of 4 pages including cover page with 4 Questions only.
2. Attempt **ALL FOUR** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please print all your answers in the Answer Booklet provided.

Question 1:

- (a) Create a truth table with input signals, S_2 , S_1 , S_0 , A , B and output signal F , of the single bit Logic Circuit shown in Table Q1.

[8 marks]

Table Q1

$S_2S_1S_0$	Logic Operation
000	$F = \bar{A}$
001	$F = AB$
010	$F = A + B$
011	$F = A \oplus B$
100	$F = \bar{B}$
101	$F = \overline{AB}$
110	$F = \overline{A + B}$
111	$F = A \oplus \bar{B}$

- (b) Based on part (a), design a single bit Logic Circuit using some standard logic gates and a 8-to-1 multiplexer.

[10 marks]

- (c) Based on part (a), design a single bit Logic Circuit using the 4-input look up table (LUT).

[7 marks]

Question 2:

Refer to the binary coded decimal (BCD) to 7-segment decoder shown in Figure Q2.1.

- (a) Construct the truth table of the binary coded decimal to 7-segment decoder to display the following characters 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, b, C, d, E and F through the 7-segment display shown in Figure Q2.2. Given that the active high 7-segment display is used with LED on = '1' and LED off = '0'.

[16 marks]

 


Figure Q2.1

 


Figure Q2.2

- (b) Design the binary coded decimal (BCD) to 7-segment display decoder shown in Figure Q2.1 using programmable logic array (PLA).


[9 marks]

Continued ...

Question 3:

- (a) Create the state assigned table of the 010 sequence recognizer shown in Figure Q3. Given that W = input signal and Z = output signal.

[5 marks]

 

- (b) Compute the simplified characteristic equations for the next state signals (X & Y) and output signal (Z) of the 010 sequence recognizer shown in Figure Q3.

[8 marks]

- (c) Design the 010 sequence recognizer shown in Figure Q3 using standard logic gates and D flip-flops.

[7 marks]

- (d) Design and sketch the state diagram of the 101 sequence recognizer.

[5 marks]

Continued ...

Question 4:

Refer to the Arithmetic and Logic Unit shown in Figure Q4.

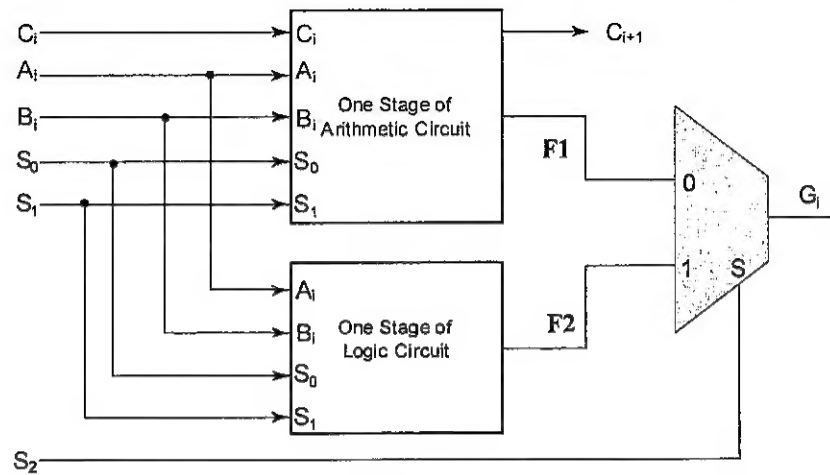


Figure Q4

Table Q4.1

$S_1 S_0$	Arithmetic Operations
00	$F1 = A \text{ plus } B$
01	$F1 = A \text{ plus } B \text{ plus } C_i$
10	$F1 = A \text{ plus } \bar{B}$
11	$F1 = A \text{ plus } \bar{B} \text{ plus } 1$

Table Q4.2

$S_1 S_0$	Logic Functions
00	$F2 = A$
01	$F2 = \bar{A}$
10	$F2 = AB$
11	$F2 = A + B$

- (a) Design a single bit full adder, with inputs C_{in} , A , B and outputs C_o , S . [15 marks]
- (b) Design a One Stage of Arithmetic Circuit shown in Figure Q4 and the truth table shown in Table Q4.1 using a single bit full adder, multiplexers and standard logic gates. [5 marks]
- (c) Design a One Stage of Logic Circuit shown in Figure Q4 with the truth table shown in Table Q4.2 using standard logic gates and multiplexer. [5 marks]

End of Paper